

2. ENTITY DESIGN

1. ENTITY =====

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity AOI is
port (A, B, C, D: in STD_LOGIC;
      F: out STD_LOGIC);
end AOI;

architecture V1 of AOI is
begin
    F <= not((A and B) or (C and D));
end V1;
```


2. SIGNAL =====

```
architecture V2 of AOI is
    signal AB, CD, O: STD_LOGIC;
begin
    AB <= A and B after 2 NS;
    CD <= C and D after 2 NS;
    O <= AB or CD after 2 NS;
    F <= not O after 1 NS;
end V2;
```

library NameLib, ... ;
use NameSubLib ... ;

entity NameEnt is
port (A, B, ... : in Type;
 F, ... : out Type);

 architecture NameA of NameEnt is
begin
 ...
end NameA;



3. COMPONENT =====

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity MUX2 is
port (SEL, A, B: in STD_LOGIC;
      F: out STD_LOGIC);
end MUX2;
```

architecture STRUCTURE of MUX2 is

```
component INV
port (A: in STD_LOGIC;
      F: out STD_LOGIC);
end component;
```


```
component AOI
port (A, B, C, D: in STD_LOGIC;
      F: out STD_LOGIC);
end component;
```

```
begin
    G1: INV port map(SEL, SELB);
    G2: AOI port map(SEL, A, SELB, B, F);
end STRUCTURE;
```

4. =====

```
G1: entity WORK.INV(ARCH)
port map (SEL, SELB);
G2: entity WORK.AOI(V2)
port map (SEL, A, SELB, B, F);
```

construiesc blocuri noi

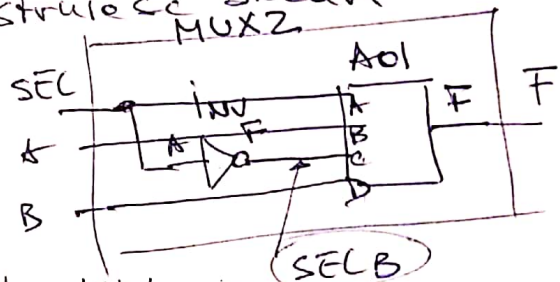

se găsește în biblioteca IEEE

declarată identic ca la entity

✓ câte comp. am atâtea port map-uri trebuie să fie

Et: Numec port map (listă legături) MUX2
{ port comp() } → { in/out Ent New }
signals

! (in/out ale noi funcțiuni, sau semnale)
Nr. elem. lista port map
Nr. elem. lista comp.

```

5. TEST BENCHES =====
library IEEE;
use IEEE.STD_LOGIC_1164.all;
(or use WORK.all;)

```

```

entity TEST_MUX4 is
end;

```

```

architecture BENCH of TEST_MUX4 is
component MUX4

```

```

port (SEL: in STD_LOGIC_VECTOR(1 downto 0);
      A, B, C, D: in STD_LOGIC;
      F: out STD_LOGIC);
end component;

```

```

signal SEL: STD_LOGIC_VECTOR(1 downto 0);
signal A, B, C, D, F: STD_LOGIC;

```

```

begin

```

```

SEL <= "00",
      "01" after 30 NS,
      "10" after 60 NS, "11" after 90 NS,
      "XX" after 120 NS, "00" after 130 NS;
A <= 'X',
  '0' after 10 NS,
  '1' after 20 NS;
B <= 'X',
  '0' after 40 NS,
  '1' after 50 NS;
C <= 'X',
  '0' after 70 NS,
  '1' after 80 NS;
D <= 'X',
  '0' after 100 NS,
  '1' after 110 NS;

```

```

M: MUX4 port map(SEL, A, B, C, D, F);

```

```

end BENCH;


```

```

configuration CFG_MUX4 of TEST_MUX4 is
for BENCH
end for;
end CFG_MUX4;

```

optional, de. e una sg.

 


-- empty entity !

coponent MUX

pot
să aibă ac. nume cu cele din component
sau NU

SEL

 

entitatea a cărei arhitecturi o selecte

numele config.

Anlit. de lectura

3. PROCESS & SYNCHRONISATION

1. PROCESS =====
architecture V3 of AOI is

```


signal AB, CD, O: STD_LOGIC;

begin
  process (A, B, C, D)
  begin
    AB <= A and B after 2 NS;
    CD <= C and D after 2 NS;
  end process;

  process (AB, CD)
  begin
    O <= AB or CD after 2 NS;
  end process;

  process (O)
  begin
    F <= not O after 1 NS;
  end process;
end V3;

```

 

process cells

-- sensitivity list !
în cadrul procesului - secvențialitate

1) - procese concurente ! 2) corp secvențial
3) se trece dacă un elem. în LS schimbă de stare = Even
4) se exec. corp. → end
= comunicare → prin signal

2. SENSITIVITY LIST

(P2:) process (SEL, A, B, C) - variabilă de sincronizare
begin

```

if SEL = '1' then
  OP <= A and MASK;
else
  OP <= B;
end if;
end process (P2);

```

© - în corp proces

MASK - în LS

proces fără LS

3. WAIT

Stimulus: process

```

begin
  Reset <= '0';
  wait for 50 NS;
  Reset <= '1';
  wait;
end process;

```

începe la t=0.

nu se atinge end process

4. TEST VECTORS

TestVectors: process - → fără listă
begin


```

A <= "0000";
B <= "0000";
wait for 10 NS;
A <= "1111";
wait for 10 NS;
B <= "1111";
wait for 10 NS;
A <= "0101";
B <= "1010";
wait;
end process;


```

1) procese concurente
corp secvențial
2) se execută la start simulare (t=0).
3) wait [for x NS]
4) → end;

 5. EVENTS
 process (A, B, S, T)
 begin
 S <= A nand B after 2 NS;
 T <= not S;
 F <= T after 1 NS;
 end process;



 6. Feedback: process (S, R, Q, QB)
 begin
 Q <= S nand QB;
 QB <= R nand Q;
 end process;



stare interz.

S	R	Q	QB
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0

= memorarea $Q_a \rightarrow Q_{anterior}$

Ex. 5

init. AB → "11" → S=0, T=1, F=1

① A → 0, { setez ev. la S } Nu se modifică
 (LS) 10 { executie → end. }

după 25 → S=1, T=1 (LS) →
 { setez ev. la T }
 { executie → end }

③ după 1 delay → T=0 10 (LS) →
 { setez ev. F }
 { executie → end }

după 1 NS F=0 10 (≠ LS)

⇒ Ft. calcule în lătruită
 în LS 3 Variabile intermediare NU - ultime